

BLG222E Computer Organization

Project 2

Due Date: 25.05.2025, 23:59

Design a **hardwired control unit** for the following architecture. Use the structure that you have designed in **Part 4 of Project 1**.

INSTRUCTION FORMAT

The instructions are stored in memory in **little-endian order**. Since the RAM in Project 1 has an 8-bit output, **the instruction register cannot be filled in one clock cycle**. You can load MSB and LSB in 2 clock cycles.

- In the first clock cycle (**T=0**), the LSB of the instruction must be loaded from an address A of the memory to the LSB of IR [i.e., IR(7-0)].
- In the second clock cycle (**T=1**), the MSB of the instruction must be loaded from an address A+1 of the memory to the MSB of IR [i.e., IR(15-8)].
- After the second clock cycle (**T=2**), the instruction starts to execute.

There are 2 types of instructions as described below.

1- Instructions with address reference have the format shown in Figure 1.

- The **OPCODE** is a **6-bit field**. (Table 1 is given for opcode definition.)
- The **RSEL** is a **2-bit field**. (Table 2 is given for register selection.)
- The **ADDRESS** is an **8-bit field**.

OPCODE (6-bit)	RSEL (2-bit)	ADDRESS (8-bit)
----------------	--------------	-----------------

Figure 1: Instructions with an address reference.

2- Instructions without an address reference have the format shown in Figure 2.

- The **OPCODE** is a **6-bit field**. (Table 1 is given for opcode definition.)
- The **DSTREG** is a **3-bit field** that specifies the destination register. (Table 3 is given.)
- The **SREG1** is a **3-bit field** that specifies the first source register. (Table 3 is given.)
- The **SREG2** is a **3-bit field** that specifies the second source register. (Table 3 is given.)
- The least significant bit is unused and have the value 0.

OPCODE (6-bit)	DSTREG(3-bit)	SREG1 (3-bit)	SREG2 (3-bit)	0
----------------	---------------	---------------	---------------	---

Figure 2: Instructions without an address reference.

Table 1: OPCODE field and symbols for operations and their descriptions.

OPCODE (HEX)	SYMBOL	DESCRIPTION
0x00	BRA	$PC \leftarrow \text{VALUE}$
0x01	BNE	IF Z=0 THEN $PC \leftarrow \text{VALUE}$
0x02	BEQ	IF Z=1 THEN $PC \leftarrow \text{VALUE}$
0x03	POPL	$SP \leftarrow SP + 1, Rx \leftarrow M[SP]$ (16-bit)
0x04	PSHL	$M[SP] \leftarrow Rx, SP \leftarrow SP - 1$ (16-bit)
0x05	POPH	$SP \leftarrow SP + 1, Rx \leftarrow M[SP]$ (32-bit)
0x06	PSHH	$M[SP] \leftarrow Rx, SP \leftarrow SP - 1$ (32-bit)
0x07	CALL	$M[SP] \leftarrow PC, SP \leftarrow SP - 1, PC \leftarrow \text{VALUE}$ (16 bit)
0x08	RET	$SP \leftarrow SP + 1, PC \leftarrow M[SP]$ (16 bit)
0x09	INC	$\text{DSTREG} \leftarrow \text{SREG1} + 1$
0x0A	DEC	$\text{DSTREG} \leftarrow \text{SREG1} - 1$
0x0B	LSL	$\text{DSTREG} \leftarrow \text{LSL SREG1}$
0x0C	LSR	$\text{DSTREG} \leftarrow \text{LSR SREG1}$
0x0D	ASR	$\text{DSTREG} \leftarrow \text{ASR SREG1}$
0x0E	CSL	$\text{DSTREG} \leftarrow \text{CSL SREG1}$
0x0F	CSR	$\text{DSTREG} \leftarrow \text{CSR SREG1}$
0x10	NOT	$\text{DSTREG} \leftarrow \text{NOT SREG1}$
0x11	AND	$\text{DSTREG} \leftarrow \text{SREG1 AND SREG2}^*$
0x12	ORR	$\text{DSTREG} \leftarrow \text{SREG1 OR SREG2}^*$
0x13	XOR	$\text{DSTREG} \leftarrow \text{SREG1 XOR SREG2}^*$
0x14	NAND	$\text{DSTREG} \leftarrow \text{SREG1 NAND SREG2}^*$
0x15	ADD	$\text{DSTREG} \leftarrow \text{SREG1} + \text{SREG2}^*$
0x16	ADC	$\text{DSTREG} \leftarrow \text{SREG1} + \text{SREG2} + \text{CARRY}^*$
0x17	SUB	$\text{DSTREG} \leftarrow \text{SREG1} - \text{SREG2}^*$
0x18	MOV	$\text{DSTREG} \leftarrow \text{SREG1}$
0x19	MOVL	$Rx[7:0] \leftarrow \text{IMMEDIATE}$ (8-bit)
0x1A	MOVSH	$Rx[31:8] \leftarrow Rx[23:0]$ (8-bit Left Shift) $Rx[7:0] \leftarrow \text{IMMEDIATE}$ (8-bit)
0x1B	LDARL	$\text{DSTREG} \leftarrow M[AR]$ (16-bit)
0x1C	LDARH	$\text{DSTREG} \leftarrow M[AR]$ (32-bit)
0x1D	STAR	$M[AR] \leftarrow \text{SREG1}$
0x1E	LDAL	$Rx \leftarrow M[\text{ADDRESS}]$ (16-bit)
0x1F	LDAH	$Rx \leftarrow M[\text{ADDRESS}]$ (32-bit)
0x20	STA	$M[\text{ADDRESS}] \leftarrow Rx$
0x21	LDDRL	$DR \leftarrow M[AR]$ (16-bit)
0x22	LDDRH	$DR \leftarrow M[AR]$ (32-bit)
0x23	STDRL	$\text{DSTREG} \leftarrow DR$
0x24	STRIM	$M[AR+\text{OFFSET}] \leftarrow Rx$ (AR is 16-bit register) (OFFSET defined in ADDRESS bits)

*To use the ARF registers for SREG2, you can load them into the scratch registers located in the RF.

Table 2: RSEL table.

RSEL	REGISTER
00	R1
01	R2
10	R3
11	R4

Table 3: DSTREG/SREG1/SREG2 selection table.

DSTREG/SREG1/SREG2	REGISTER
000	PC
001	SP
010	AR
011	AR
100	R1
101	R2
110	R3
111	R4

SIMPLE EXAMPLE

Since the PC value is initially 0, your code first executes the instruction in memory address 0x00. This instruction is BRA START_ADDRESS where START_ADDRESS is the starting address of your instructions.

You have to determine the binary code of the program and write it to memory. Your final Verilog implementation is expected to fetch the instructions starting from address 0x00, decode them, and execute all instructions one by one.

```

        BRA    0x18          # This instruction is written to the memory address 0x00,
                                # The first instruction must be written to address 0x18

        MOVL   R1, 0x00      # R1 is used for iteration number
        MOVSH  R1, 0x06

        MOVL   R2, 0x00      # R2 is used to store total
        MOVL   R3, 0xB0

        MOV    AR, R3        # AR is used to track data address: starts from 0xB0
LABEL:   LDARH  R4            # R3 ← M[AR] (reads 32-bits)
        ADD    R2, R2, R4    # R2 ← R2 + R3 (Total = Total + M[AR])
        INC    AR, AR        # AR ← AR + 1 (Next Data)
        DEC    R1, R1        # R1 ← R1 – 1 (Decrement Iteration Counter)
        BNE    LABEL        # Go back to LABEL if Z=0 (Iteration Counter > 0)
        INC    AR, AR        # AR ← AR + 1 (Total will be written to 0xC9)
        STAR   R2            # M[AR] ← R2 (Store Total at 0xC9)

```

Note: CPU System Simulation code will be shared later.

Submission:

Implement your design in Verilog HDL, and upload a single compressed (zip) file to Ninova before the deadline. Only one student from each group should submit the project files (select one member of the group as the group representative for this purpose and note his/her student ID). Example submission file and module name declarations are given as attachments. This compressed file should contain your modules file (.v) for each part, the given simulation file (.v), and a report that contains:

- the number & names of the students in the group
- information about your control unit design
- count of clock cycles each instruction takes
- count of clock cycles given code snippet takes
- task distribution of each group member

Group work is expected for this project. All members of the group must design together. You must ensure that all modules work properly. After designing your project, you can check your results by running the given simulation files. You are expected to get results by running the given .bat file. **The project will be evaluated only using simulation files. There will not be any partial grading for the designs. If your codes get any error, you will not get any grades for that part so make sure that your codes are working with the given simulation files. There will not be any demonstration sessions.** You can ask your questions through the **Message Board**, so do not ask questions through email.